

EEE 304 – Digital Electronics Laboratory

July 2022 Level-3 Term-II Section C2

Final Project Demonstration

Water Level Indicator Using 74 Series IC and 7 Segment Display

SUBMITTED BY – GROUP C2.04



Moytri Ghosal
1806167



Sandipa Chowdhury
1806168



Sudipto Pramanik
1806172




Tusher Karmakar
1806174



BANGLADESH UNIVERSITY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Outline

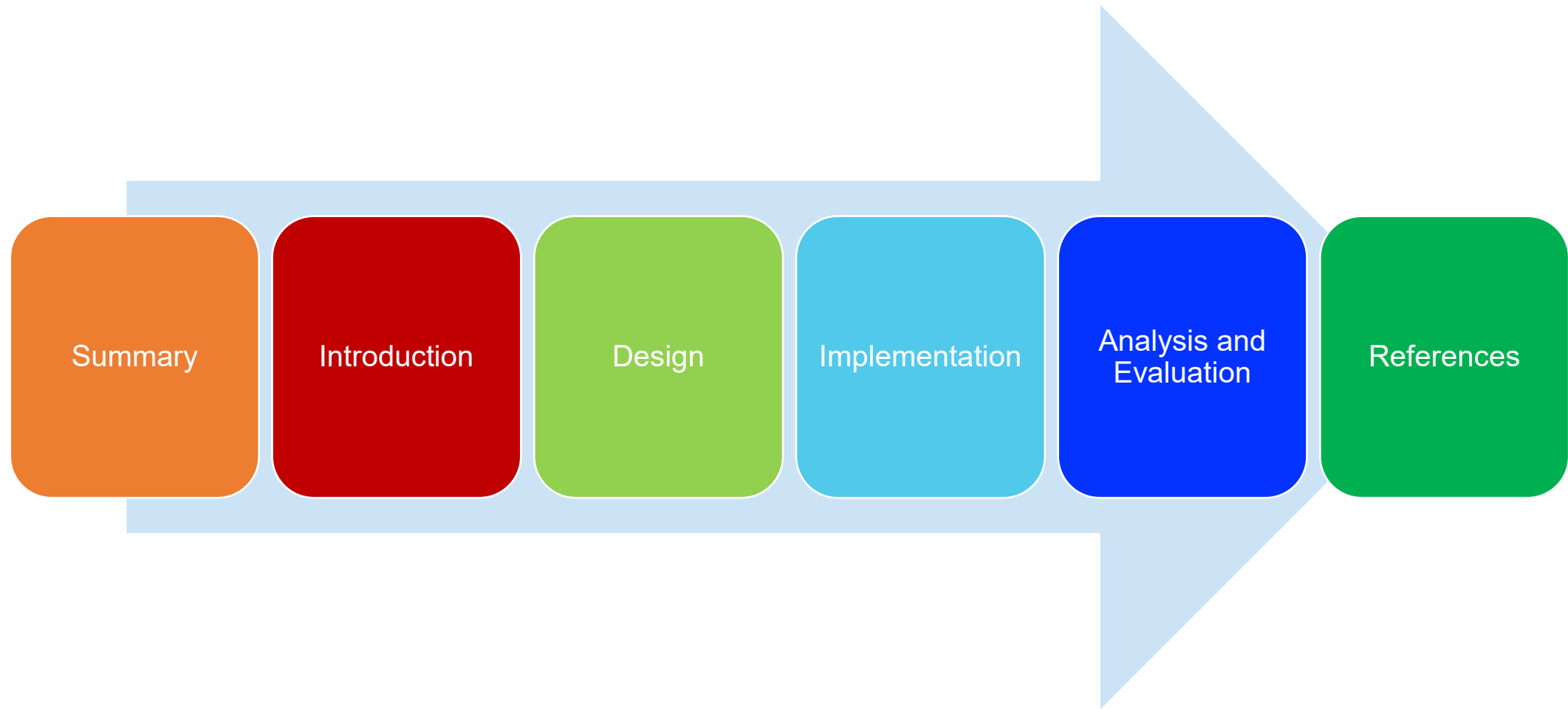

Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration

Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration


Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



1. Summary

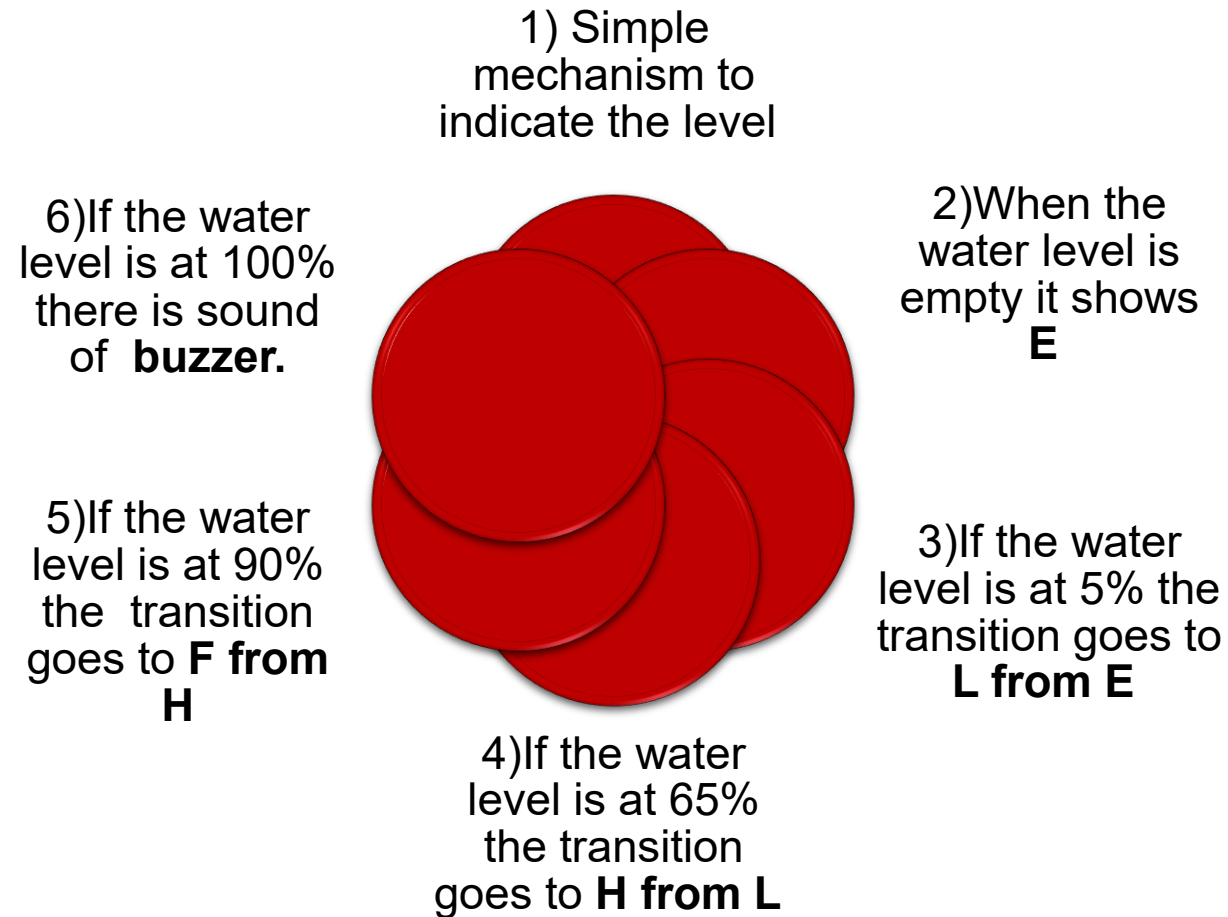

Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration

Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References




2. Introduction

Designed to deal with the water level problem using basic logic ICs.


Small in size

Can be used in factories, households , water storage tanks .

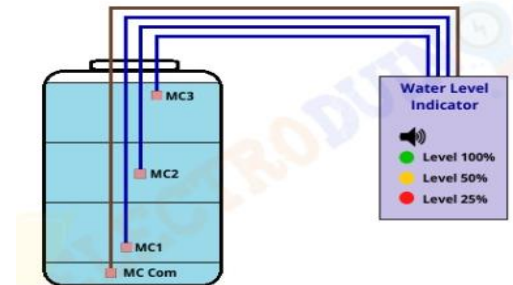Further modification can also be made it possible as flood indicator.




2.1 Complexity Analysis

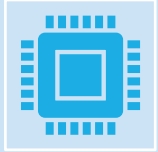

Can be further modified with automated on-off system .



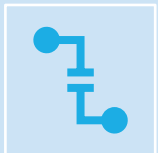The water here can be a source of conductance .



If BJTs are used then this characteristics of water will be used to switch on /off these as switches .

Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design


Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



3.1 Design: Circuit Diagram(simulation)

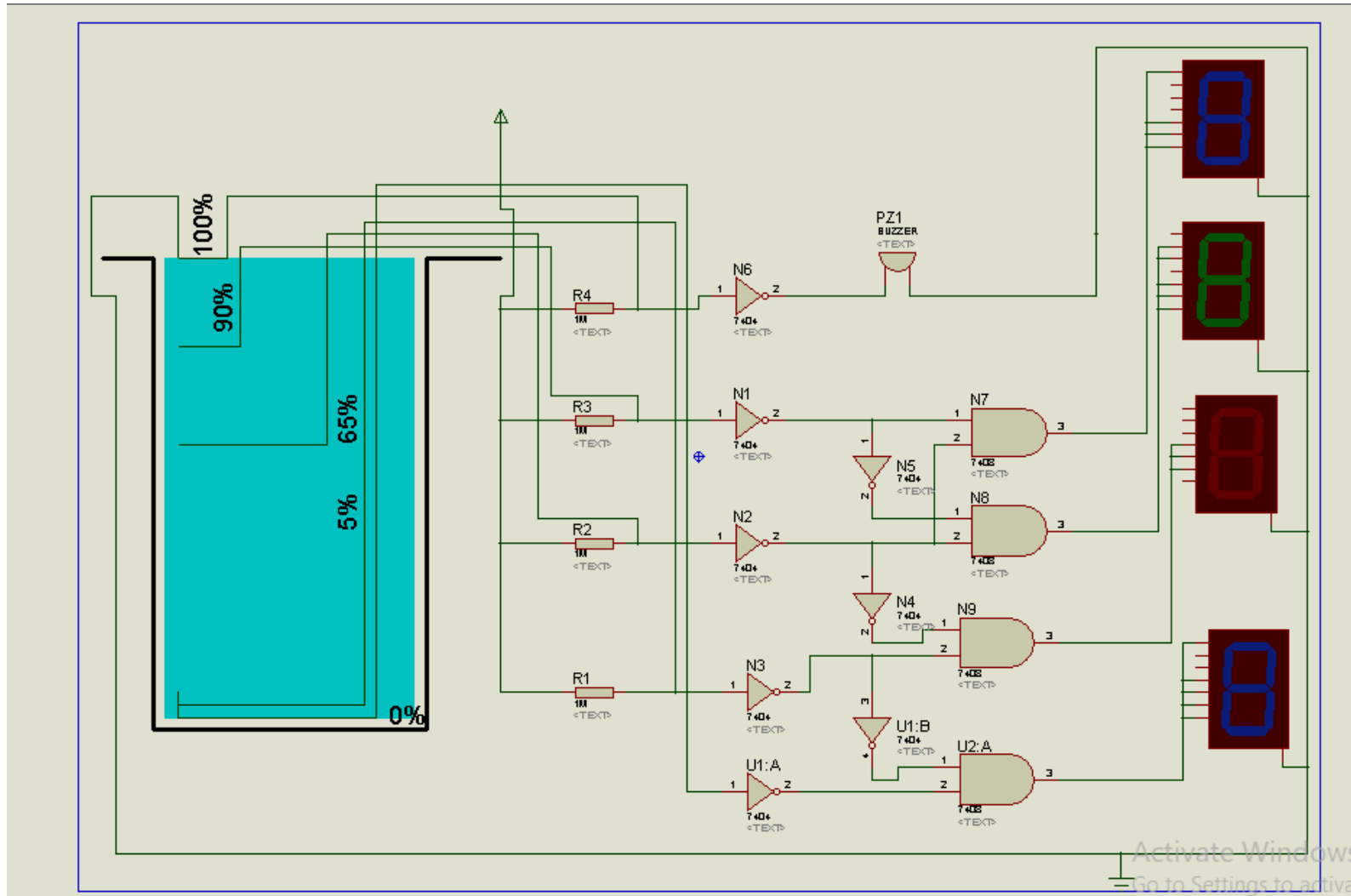

3.2 Design: Methods

Components used :

1) 7404 Ics

2)7408 ICs


3) Test-tube

4)Wires

5) Seven segment display.




Design: Methods(When Tank Is Empty)

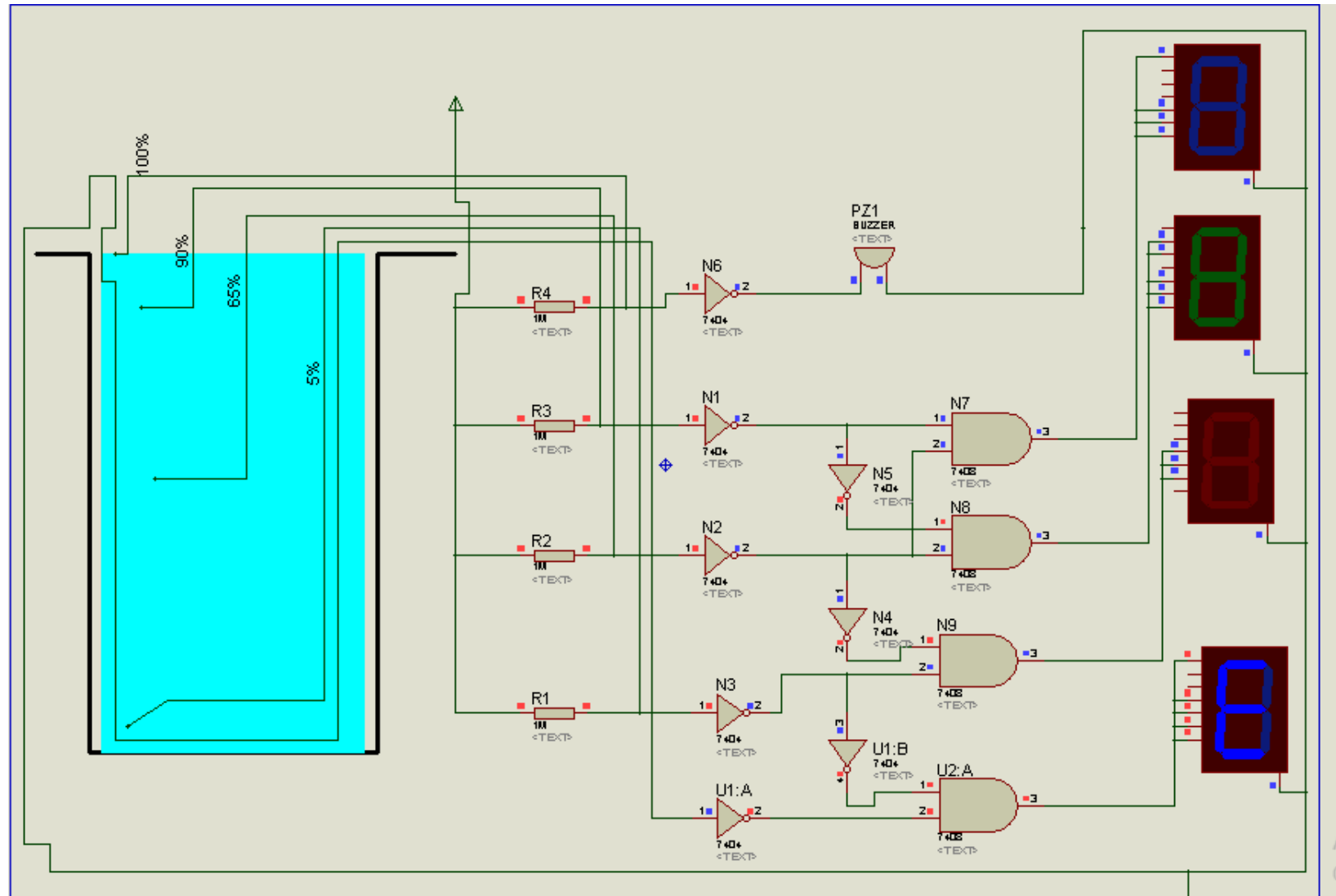





Design: Methods(When Tank Is High)

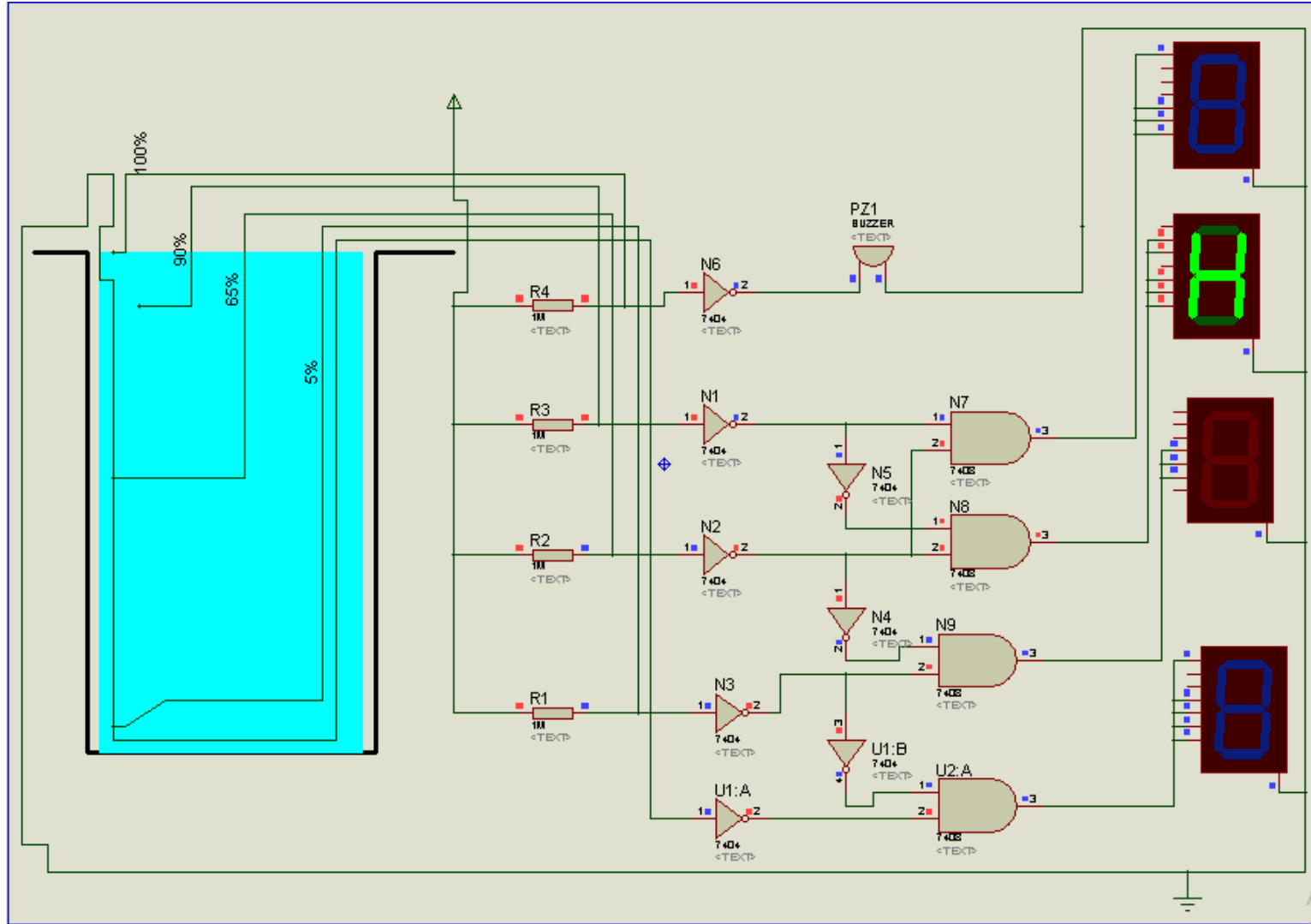






Design:Methods(When Tank Is Full)

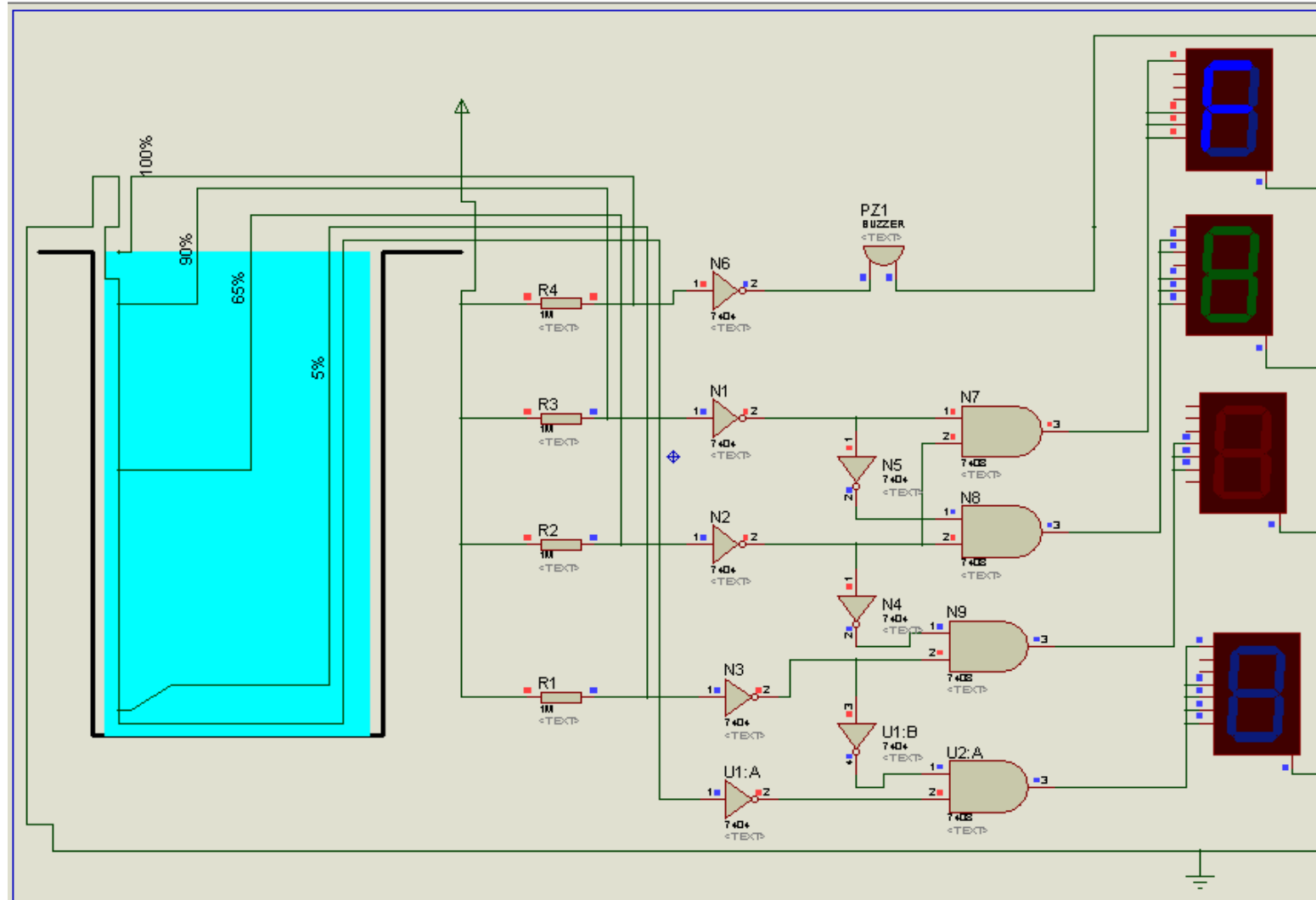


Design: Methods(When Tank Is Overflowed)

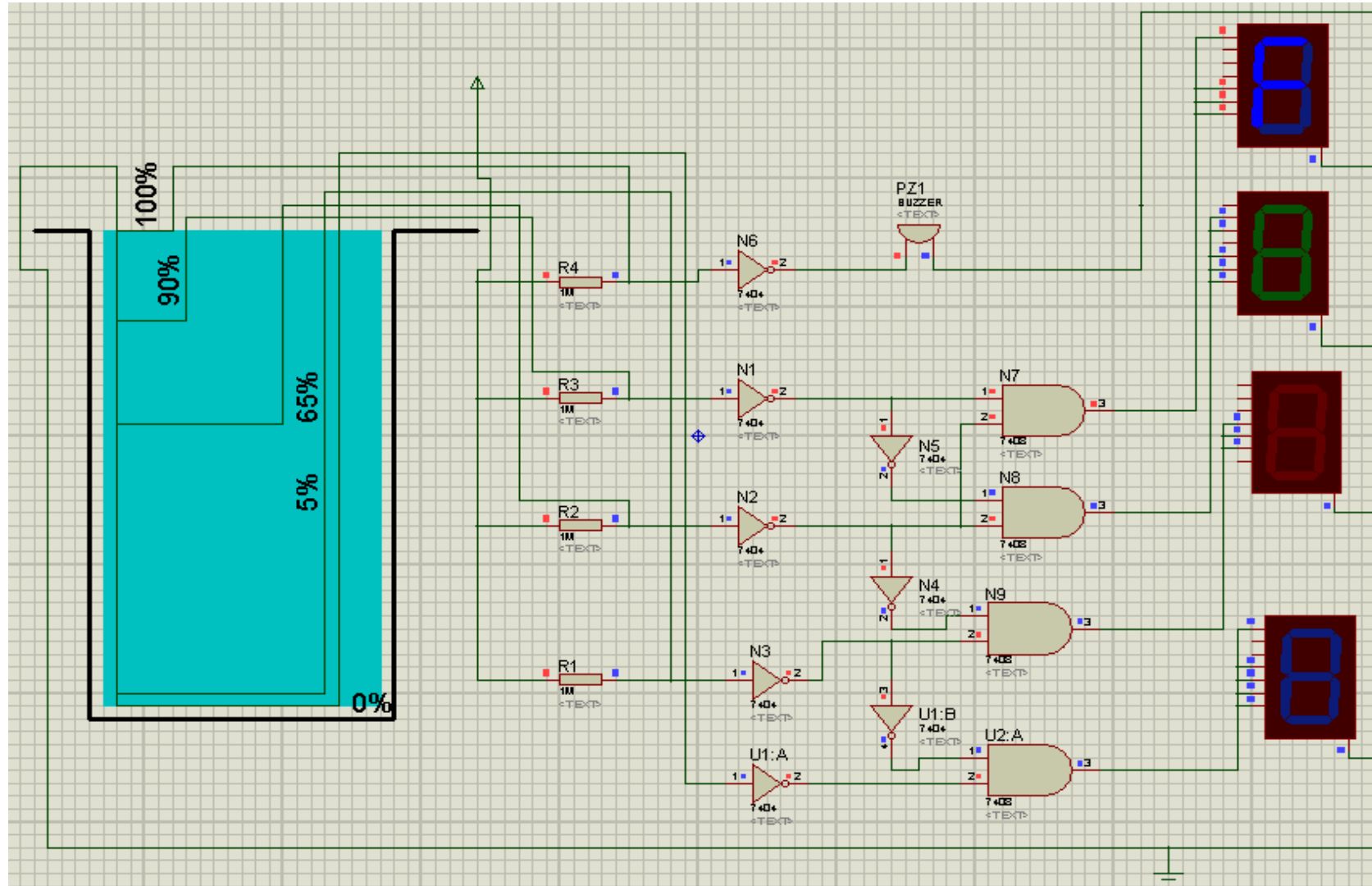

3.4.1 Implementation: Photo Gallery

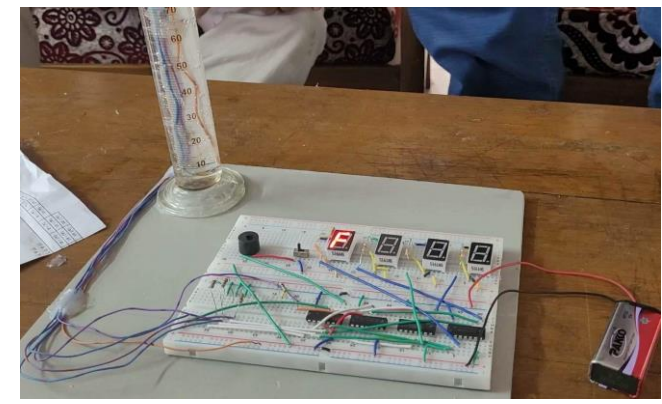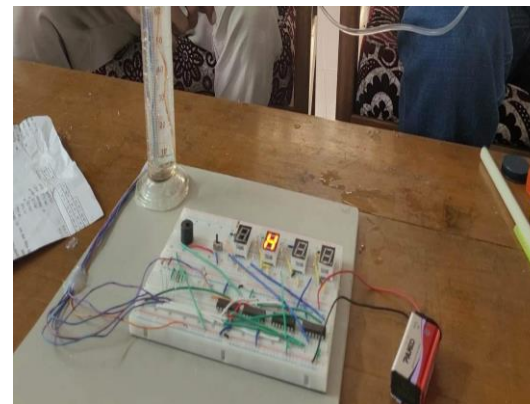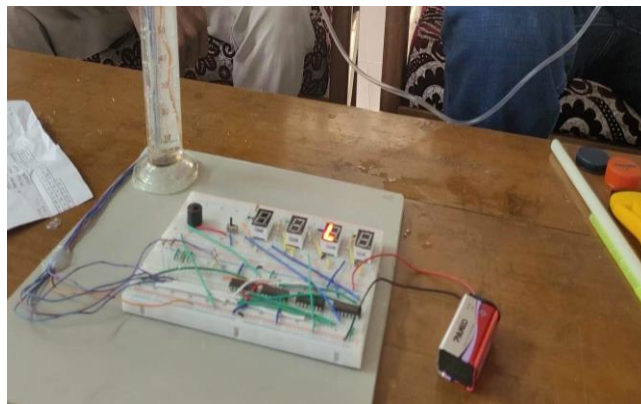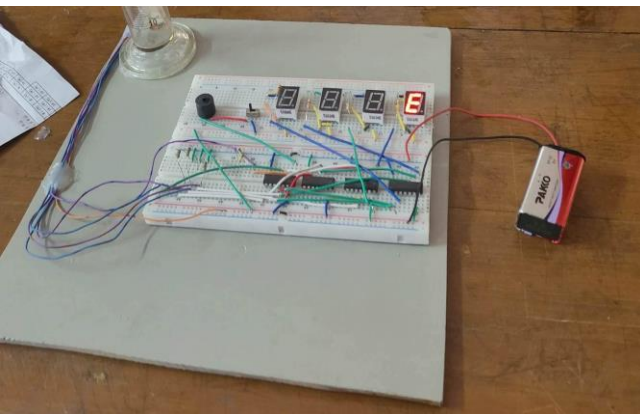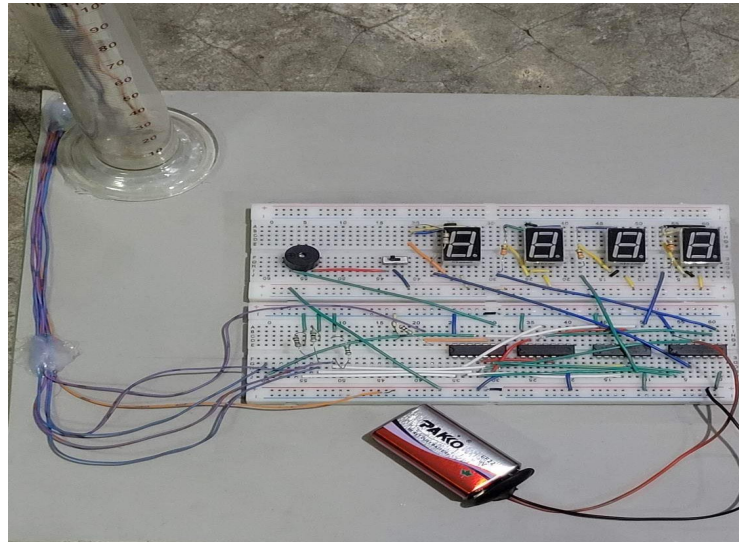


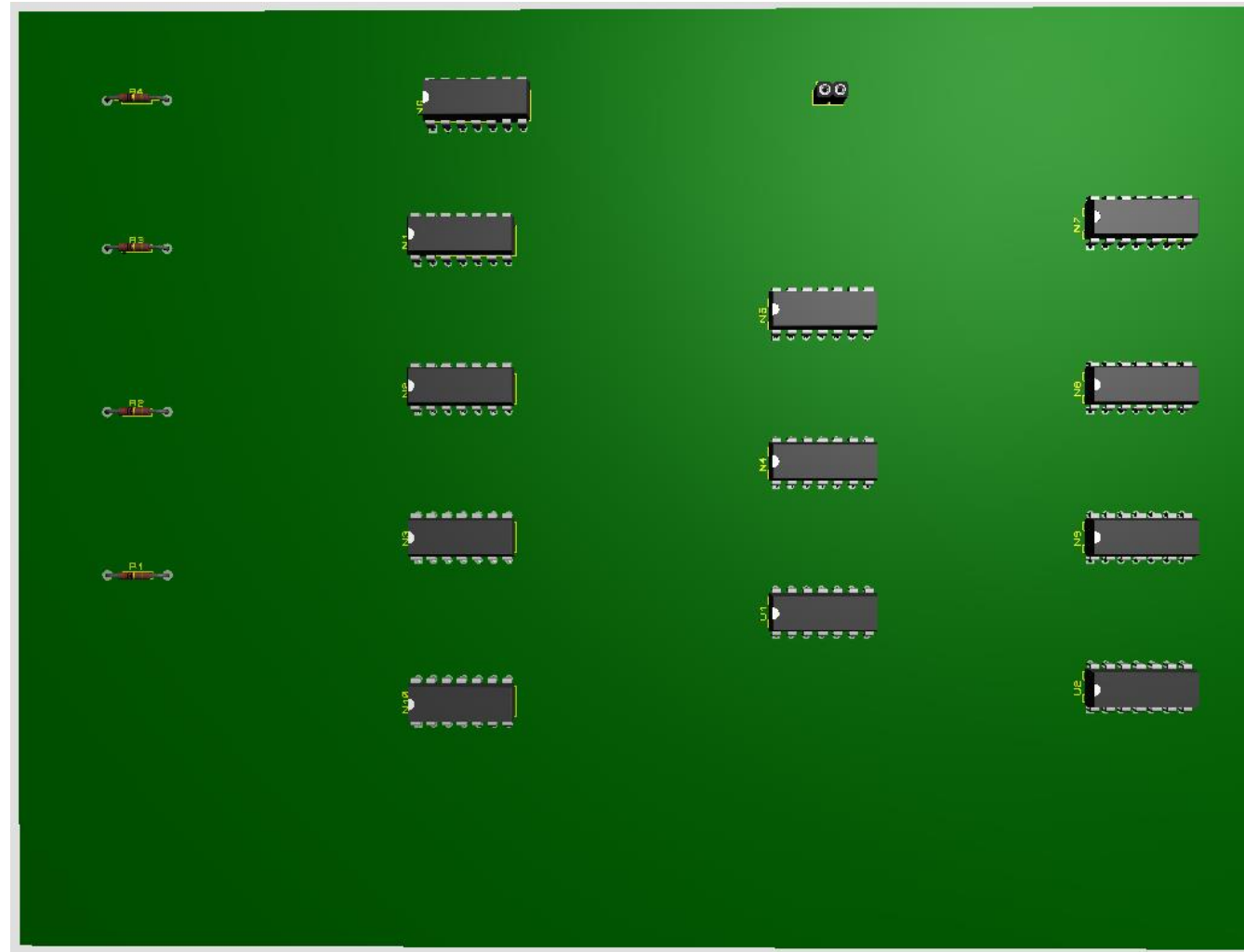3.4.2 Design: PCB Layout and 3d rendering







3.5 Simulation Results / Bench Mark

- Presented by: 1806172

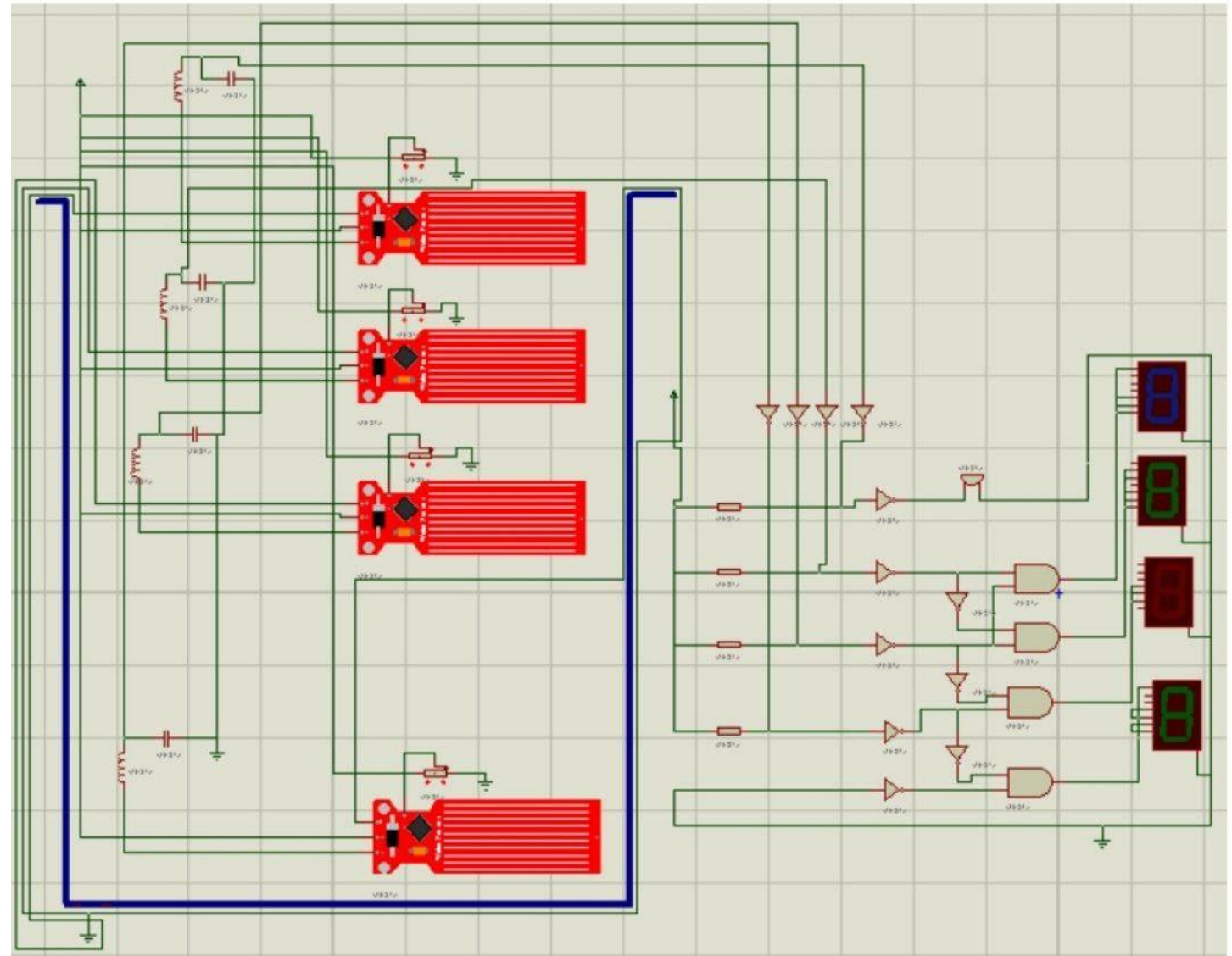

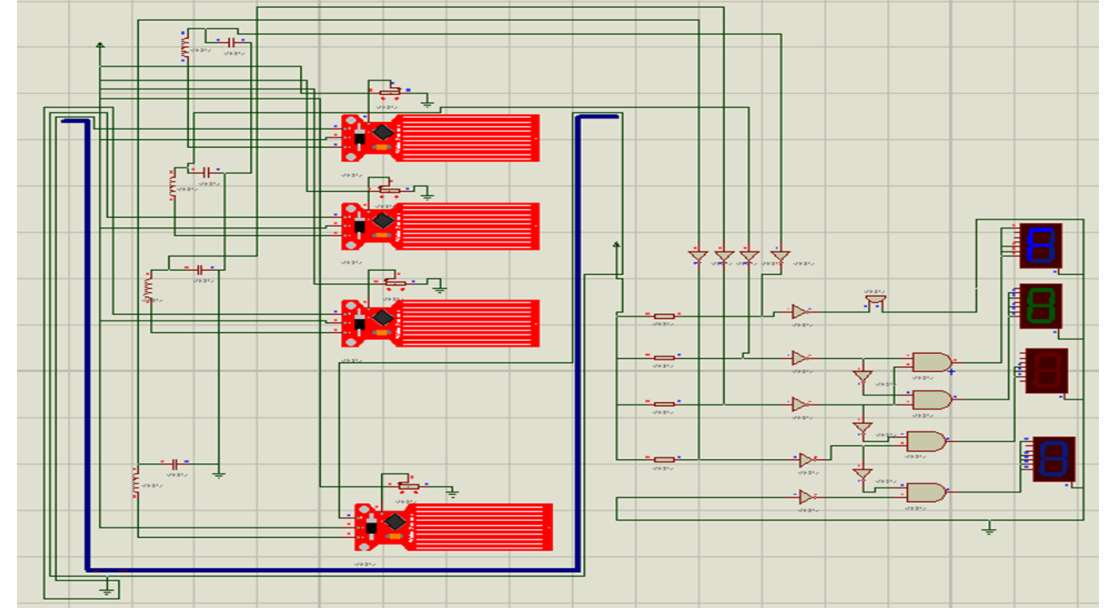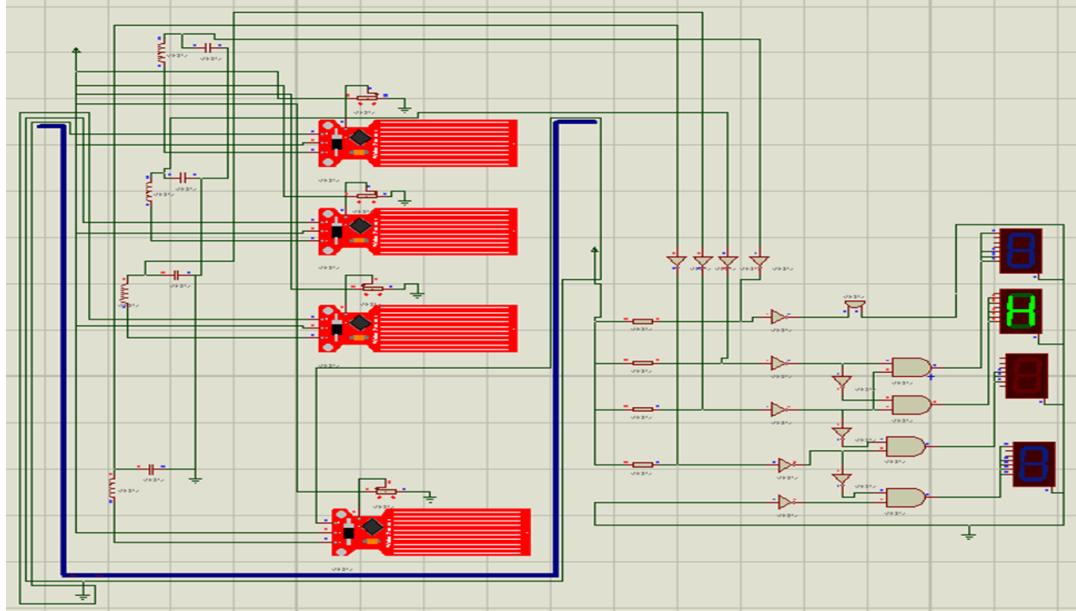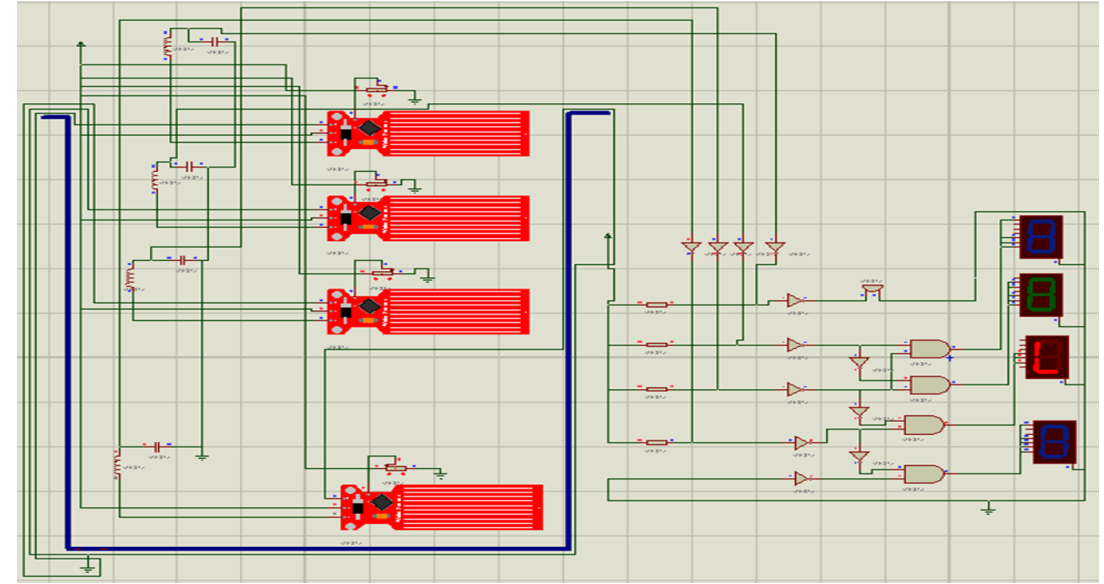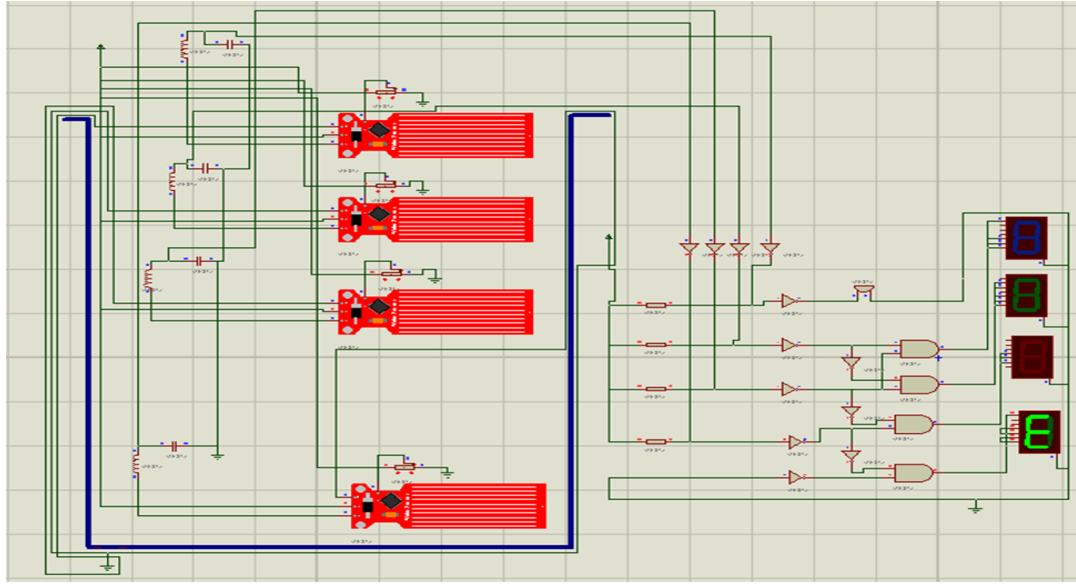Water Level Inductor Using 74 Series IC and 7 Segment Display



Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration

Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



Demonstration Video

- <https://youtu.be/Qdus7yexIbQ>



Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration

Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



4. Limitations and Practical Considerations

4.1 Limitations

- Didn't use water level sensor
- It's a miniature version

4.2.1 Practical Considerations: Public Health and Safety

Observing water level in



1)water treatment plants



2)Swimming pools

4.2.2 Practical Considerations: Environment

Observation of water level in:



```
graph TD; A[Observation of water level in:] --> B[1) Aquariums]; B --> C[2) Agricultural irrigation system]
```

1) Aquariums

2) Agricultural irrigation system



Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration


Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



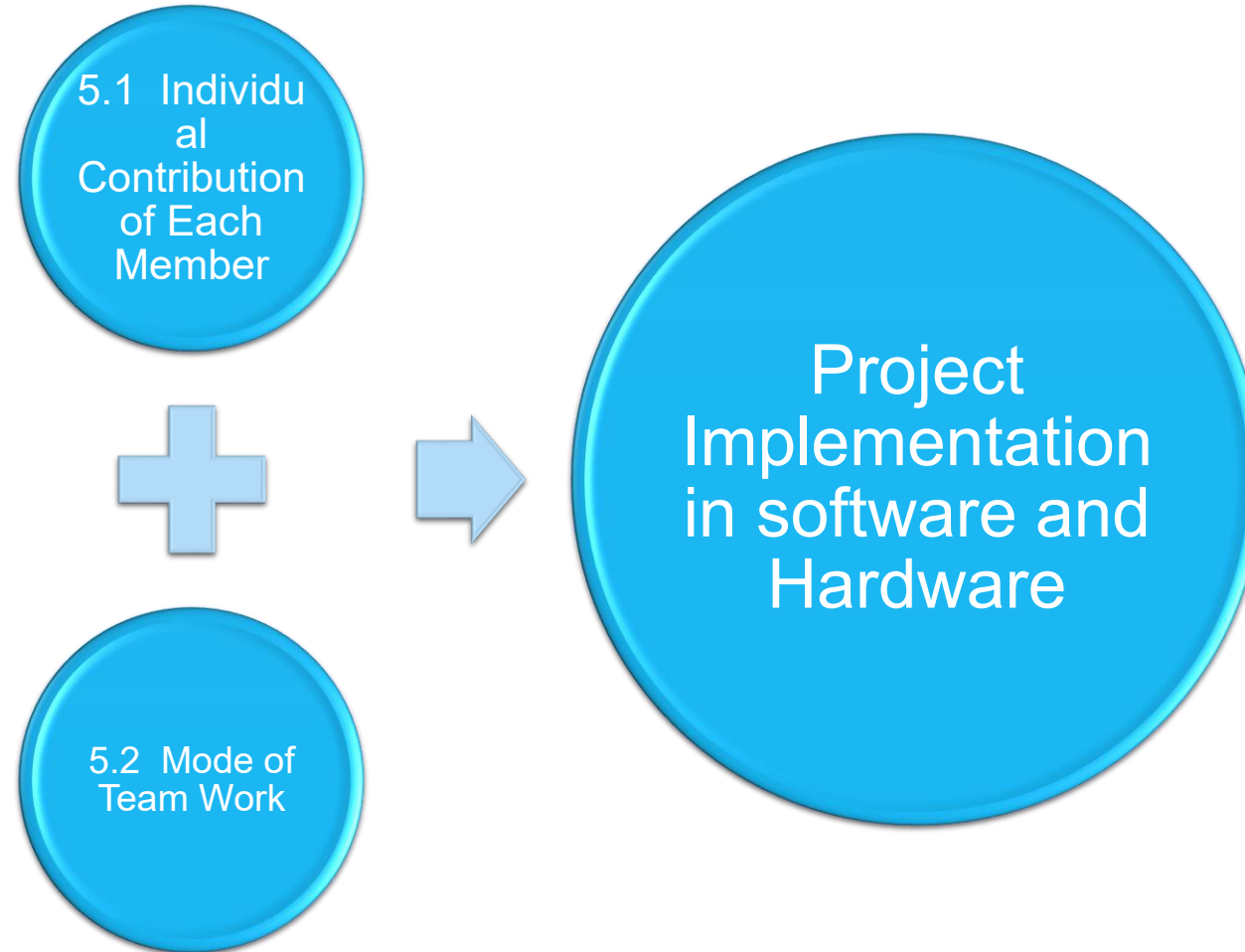5. Reflection on Individual and Team work



5.1 Individual Contribution of Each Member


Two of us did
simulation
Proteus &
Tinkercad

Everybody was
present in
circuit
implementation

Remaining two
added new
feature like
buzzer



5.2 Mode of team work

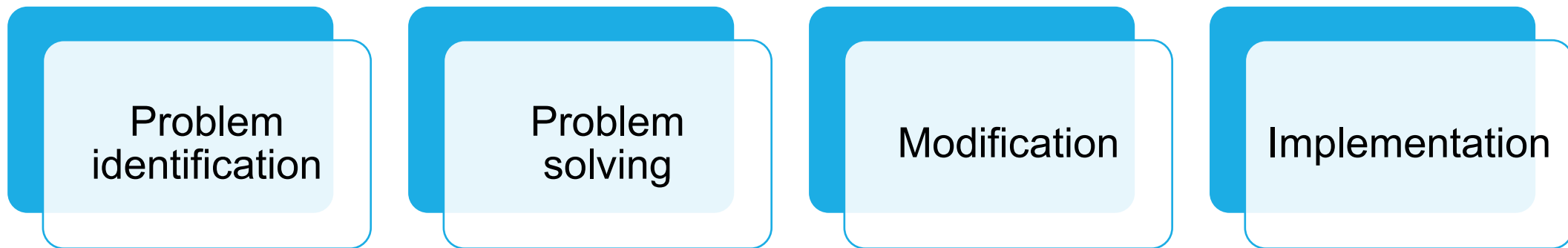

Water Level Indicator Using 74 Series IC and 7 Segment Display

Summary

Introduction

Technical Details of Design

Demonstration

Limitations and Practical Considerations

Reflection on Individual and Teamwork

Acknowledgement and References



6. References

- **Reference:**

<https://www.circuitstoday.com/water-level-controller-using-arduino>

<https://github.com/iamvishalprasad/Water-Level-Controller-using-8051-Microcontroller>

